

# cs113 Lab2: By Amuldeep Dhillon

---

Text written to file build.sh

```
| doctex lab.doc  
| pptexenv latex lab.tex  
| dvipdf lab.dvi
```

Bourne Shell


```
| chmod 777 build.sh  
| ./build.sh
```

$P$	$\sim P$
0	1
1	0

SML

```
exception Error;  
fun NOT(0) = 1 | NOT(1) = 0 | NOT(_) = raise Error;  
val truthValues1 = [(0),(1)];  
map NOT truthValues1;
```

```
> exception Error;  
fun NOT(0) = 1 | NOT(1) = 0 | NOT(_) = raise Error;  
val truthValues1 = [(0),(1)];  
map NOT truthValues1;  
exception Error  
> val NOT = fn: int -> int  
> val truthValues1 = [0, 1]: int list  
> val it = [1, 0]: int list
```

 

NOT gate

$$R \equiv \sim P$$


## cs113 Lab2: And Gate

$P$	$Q$	$P \wedge Q$
0	0	0
0	1	0
1	0	0
1	1	1

SML

```
exception Error;  
fun AND(0,_) = 0 | AND(1,x) = x | AND(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map AND truthValues2;
```

```
> exception Error;  
fun AND(0,_) = 0 | AND(1,x) = x | AND(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map AND truthValues2;  
exception Error  
> val AND = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [0, 0, 0, 1]: int list
```

 

AND gate

$$R \equiv P \wedge Q$$


## cs113 Lab2: Or Gate

$P$	$Q$	$P \vee Q$
0	0	0
0	1	1
1	0	1
1	1	1

SML

```
exception Error;  
fun OR(1,_) = 1 | OR(0,x) = x | OR(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map OR truthValues2;
```

```
> exception Error;  
fun OR(1,_) = 1 | OR(0,x) = x | OR(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map OR truthValues2;  
exception Error  
> val OR = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [0, 1, 1, 1]: int list
```

 

$$R \equiv P \vee Q$$


## cs113 Lab2: Nand Gate

$P$	$Q$	$P \mid Q$
0	0	1
0	1	1
1	0	1
1	1	0

SML

```
exception Error;  
fun NAND(0,_) = 1 | NAND(1,x) = NOT(x) | NAND(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map NAND truthValues2;
```

```
> exception Error;  
> fun NAND(0,_) = 1 | NAND(1,x) = NOT(x) | NAND(_,_) = raise Error;  
> val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
> map NAND truthValues2;  
exception Error  
> val NAND = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [1, 1, 1, 0]: int list
```

 

$$R \equiv P \mid Q$$


## cs113 Lab2: Nor Gate

$P$	$Q$	$P \downarrow Q$
0	0	1
0	1	0
1	0	0
1	1	0

SML

```
exception Error;  
fun NOR(1,_) = 0 | NOR(0,x) = NOT(x) | NOR(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map NOR truthValues2;
```

```
> exception Error;  
fun NOR(1,_) = 0 | NOR(0,x) = NOT(x) | NOR(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map NOR truthValues2;  
exception Error  
> val NOR = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [1, 0, 0, 0]: int list
```

 

NOR gate

$$R \equiv P \downarrow Q$$


## cs113 Lab2: Xor Gate

$P$	$Q$	$P \oplus Q$
0	0	0
0	1	1
1	0	1
1	1	0

SML

```
exception Error;  
fun XOR(0,x) = x | XOR(1,x) = NOT(x) | XOR(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map XOR truthValues2;
```

```
> exception Error;  
fun XOR(0,x) = x | XOR(1,x) = NOT(x) | XOR(_,_) = raise Error;  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map XOR truthValues2;  
exception Error  
> val XOR = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [0, 1, 1, 0]: int list
```

 

$$R \equiv P \oplus Q$$

## cs113 Lab2: Problem 2.1

- Example 2.2 truth table and circuit


$P$	$Q$	$R$	$((P \vee Q) \wedge (P \vee R))$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

SML

```
fun ex22(P,Q,R) = AND(OR(P,Q),OR(P,R));  
val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
(1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map ex22 truthValues3;
```

```
> fun ex22(P,Q,R) = AND(OR(P,Q),OR(P,R));  
val truthValues3 =  
[(0,0,0),(0,0,1),(0,1,0),(0,1,1),(1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map ex22 truthValues3;  
val ex22 = fn: int * int * int -> int  
> val truthValues3 =  
  [(0, 0, 0), (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1),  
   (1, 1, 0), (1, 1, 1)]: (int * int * int) list  
> val it = [0, 0, 0, 1, 1, 1, 1, 1]: int list
```
 
$$S \equiv ((P \vee Q) \wedge (P \vee R))$$





## cs113 Lab2: Problem 2.2

- Circuit of  $((P \wedge Q) \vee \sim R)$


$P$	$Q$	$R$	$((P \wedge Q) \vee \sim R)$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

```
> fun p22(P,Q,R) = OR(AND(P,Q),NOT(R));  
val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
  (1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map p22 truthValues3;  
val p22 = fn: int * int * int -> int  
> # val truthValues3 =  
  [(0, 0, 0), (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1),  
    (1, 1, 0), (1, 1, 1)]: (int * int * int) list  
> val it = [1, 0, 1, 0, 1, 0, 1, 1]: int list
```

SML

```
| fun p22(P,Q,R) = OR(AND(P,Q),NOT(R));  
| val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
| (1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
| map p22 truthValues3;
```

$$S \equiv ((P \wedge Q) \vee \sim R)$$

 

## cs113 Lab2: Problem 2.3

- Match the figure in the Book for Problem 2.3

$P$	$Q$	$R$	$S$	$(P \wedge Q) \wedge (\sim R)$
1	1	1	0	0
1	1	0	1	1
1	0	1	0	0
1	0	0	0	0
0	1	1	0	0
0	1	0	0	0
0	0	1	0	0
0	0	0	0	0


```
> fun p23(P,Q,R) = AND(AND(P,Q),NOT(R));  
val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
  (1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map p23 truthValues3;  
val p23 = fn: int * int * int -> int  
> # val truthValues3 =  
  [(0, 0, 0), (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1),  
    (1, 1, 0), (1, 1, 1)]: (int * int * int) list  
> val it = [0, 0, 0, 0, 0, 0, 1, 0]: int list
```

$$S \equiv ((P \wedge Q) \wedge \sim R)$$

- Since the last two columns are identical  
(Left from textbook), they are equivalent

SML

```
| fun p23(P,Q,R) = AND(AND(P,Q),NOT(R));  
| val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
| (1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
| map p23 truthValues3;
```

 

## cs113 Lab2: Problem 2.7

- Create the Truth Table for the given Circuit for Problem 2.7


$P$	$Q$	$R$	$(P \wedge \sim Q) \vee (Q \wedge R)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

```
> fun p27(P,Q,R) = OR(AND(P,NOT(Q)),AND(Q,R));  
val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
(1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map p27 truthValues3;  
val p27 = fn: int * int * int -> int  
> # val truthValues3 =  
    [(0, 0, 0), (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1),  
     (1, 1, 0), (1, 1, 1)]: (int * int * int) list  
> val it = [0, 0, 0, 1, 1, 1, 0, 1]: int list
```

$$S \equiv (P \wedge \sim Q) \vee (Q \wedge R)$$

SML
 
```
fun p27(P,Q,R) = OR(AND(P,NOT(Q)),AND(Q,R));  
val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
(1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map p27 truthValues3;
```



## cs113 Lab2: Problem 2.8

- Create the Truth Table for the exclusive nor for Problem 2.8


$P$	$Q$	$\sim (P \oplus Q)$
0	0	1
0	1	0
1	0	0
1	1	1

```
> fun p28(P,Q) = NOT(XOR(P,Q));  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map p28 truthValues2;  
val p28 = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [1, 0, 0, 1]: int list
```

SML

```
fun p28(P,Q) = NOT(XOR(P,Q));  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map p28 truthValues2;
```

$$S \equiv \sim (P \oplus Q)$$

 

## cs113 Lab2: Problem 2.10

- Create the Circuit for the given Boolean Function for Problem 2.10


$P$	$Q$	$R$	$((P \wedge Q) \vee ((Q \wedge R) \wedge (Q \vee R)))$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

```
> fun p210(P,Q,R) = OR(AND(P,Q),AND(AND(Q,R),OR(Q,R)));  
val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
(1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map p210 truthValues3;  
val p210 = fn: int * int * int -> int  
> # val truthValues3 =  
    [(0, 0, 0), (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1),  
     (1, 1, 0), (1, 1, 1)]: (int * int * int) list  
> val it = [0, 0, 0, 1, 0, 0, 1, 1]: int list
```

$$S \equiv ((P \wedge Q) \vee ((Q \wedge R) \wedge (Q \vee R)))$$

SML
 
```
fun p210(P,Q,R) = OR(AND(P,Q),AND(AND(Q,R),OR(Q,R)));  
val truthValues3 = [(0,0,0),(0,0,1),(0,1,0),(0,1,1),  
(1,0,0),(1,0,1),(1,1,0),(1,1,1)];  
map p210 truthValues3;
```





## cs113 Lab2: Problem 2.14

- Prove the two Circuits are equivalent for Problem 2.14

$P$	$Q$	$((P \wedge Q) \vee (\sim P \wedge \sim Q))$
0	0	1
0	1	0
1	0	0
1	1	1

$P$	$Q$	$\sim (P \oplus Q)$
0	0	1
0	1	0
1	0	0
1	1	1

  - Since the last column of both tables are identical the two expressions are equivalent



## cs113 Lab2: Problem 2.14 (Cont.)

- Prove the two Circuits are equivalent for Problem 2.14

SML

```
fun p214a(P,Q) = OR(AND(P,Q),AND(NOT(P),NOT(Q)));  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map p214a truthValues2;
```

```
> fun p214a(P,Q) = OR(AND(P,Q),AND(NOT(P),NOT(Q)));  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map p214a truthValues2;  
val p214a = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [1, 0, 0, 1]: int list
```

$$(P \wedge Q) \vee (\sim P \wedge \sim Q) \equiv \sim (P \oplus Q)$$

```
fun p214b(P,Q) = NOT(XOR(P,Q));  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map p214b truthValues2;
```

```
> fun p214b(P,Q) = NOT(XOR(P,Q));  
val truthValues2 = [(0,0),(0,1),(1,0),(1,1)];  
map p214b truthValues2;  
val p214b = fn: int * int -> int  
> val truthValues2 = [(0, 0), (0, 1), (1, 0), (1, 1)]: (int * int) list  
> val it = [1, 0, 0, 1]: int list
```